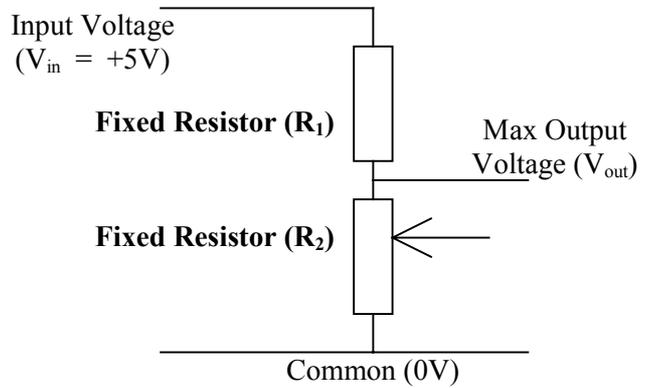


Using potentiometers as sensors.

*"The MIDIcreator has a 5V output, but the proportional inputs are 0-3.2V.
How do I connect a potentiometer to the proportional inputs?"*

This can be done by using an additional, fixed, resistor to set the maximum output voltage, from the potentiometer.
The output voltage is determined by the *ratio* of the two resistors in the chain.
In this example, the output voltage V_{out} is

$$\text{given by: } V_{out} = \frac{R_2}{R_1 + R_2} V_{in} \quad \dots(1)$$




How do I select the value of R_1 ?

The value of R_1 should be chosen so as to give a voltage of 3.2V at point "A".
As the potentiometer is moved a voltage of between 0 and 3.2V is presented to the MIDIcreator input ¹.

For example:

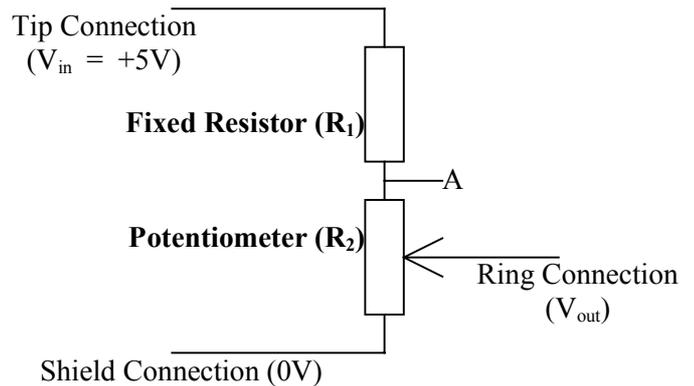If a 10K Ω potentiometer is to be used, to give a voltage of between 0 and 3.2V at the input to MIDIcreator.



$$\text{Re-arranging equation (1) gives us : } R_1 = \left(\frac{V_{in}}{V_{out}} - 1 \right) R_2 = \left(\frac{5}{3.2} - 1 \right) 10K\Omega = 5.625 K\Omega$$

The nearest "standard" value of resistor is 5.6K Ω , giving a voltage range of 0 - 3.205V ².

¹ The input impedance of the MIDIcreator is 100K Ω to ground. If the potentiometer is of too large a value, this impedance must be taken into account, and the resultant voltage range produced by the potentiometer will be non-linear.

² It is best to produce a maximum voltage of at least 3.2V, in order to utilise the full range of the MIDIcreator proportional input. Hence selecting a value of R_1 which is LESS THAN the calculated value.